

Project 4: SRAM

Computer Organization CSC 34300 - EF

By: Sebastian Grygorczuk

## Tabel of Content:

Objective.....	2
Part 1: Fundamentals.....	2
SR-Latch.....	2
Control SR-Latch.....	3
D-Latch.....	5
Master Slave Flip Flop.....	6
Part 2: SRAM:.....	7
SRAM Cell.....	7
SRAM 16x1 Module.....	8
Address Decoder.....	10
SRAM 16x4.....	12
Seven Segment Display.....	13
SRAM 16x4 and 16x8 With Seven Segment Display.....	16
SRAM 16x32.....	16
Conclusion.....	20

## Objective:

The objective of this lab is to create a 16x32 SRAM and display the results of it on eight seven segment displays using eight bit input, four bit address operation code, chip select input, write enable input and output enable input and four keys to select which eight bits to of the address to write to.

## Fundamentals:

Before we start working on building a memory we have to go over some basic elements that will help us to build towards the SRAM, these elements are SR-Latch, Control SR-Latch, D-Latch, and the Master Slave Flip Flop.

### SR-Latch

The SR-Latch, is a basic memory device, it has two inputs Set and Reset which define the output if Q and Q' to be [1,0] when S is 1 and R is 0, and [0,1] when S is 0 and R is 1. When both are zero the SR-Latch will hold the value that was computed before, and when the two are both 1 the output is unpredictable and for such reason SR-Latch requires improvement we will see with the following devices. Below is the implementation of SR-Latch in Block Diagram and it's waveform.

S	R	Q	Q'	State
0	0	Q	Q'	No Change
0	1	0	1	Reset
1	0	1	0	Set
1	1	?	?	Undefined

Tabel 1. SR-Latch Truth Table

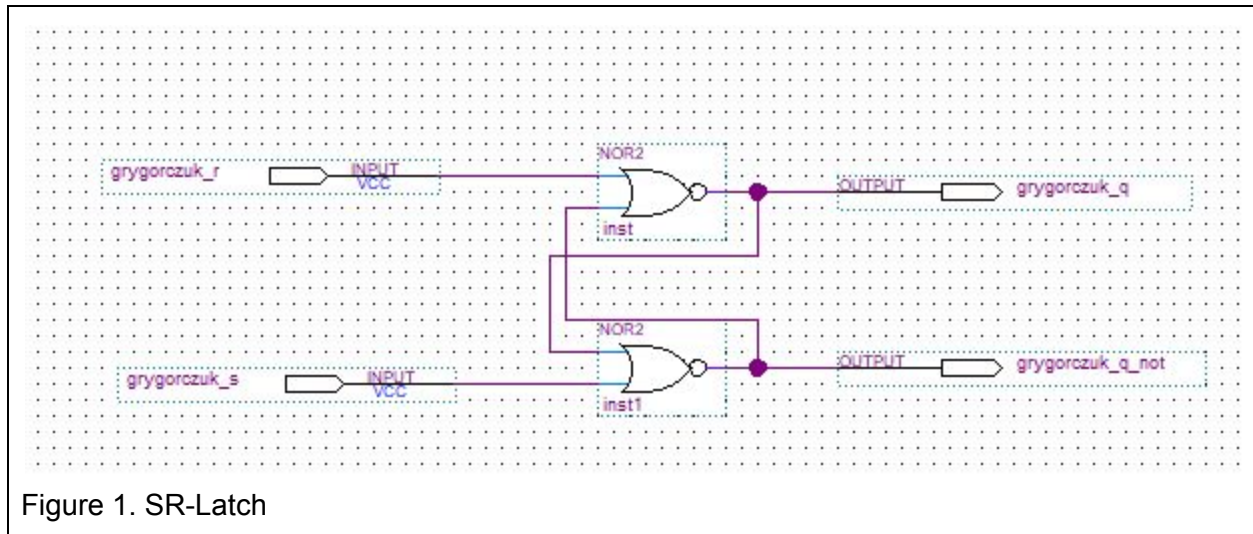


Figure 1. SR-Latch

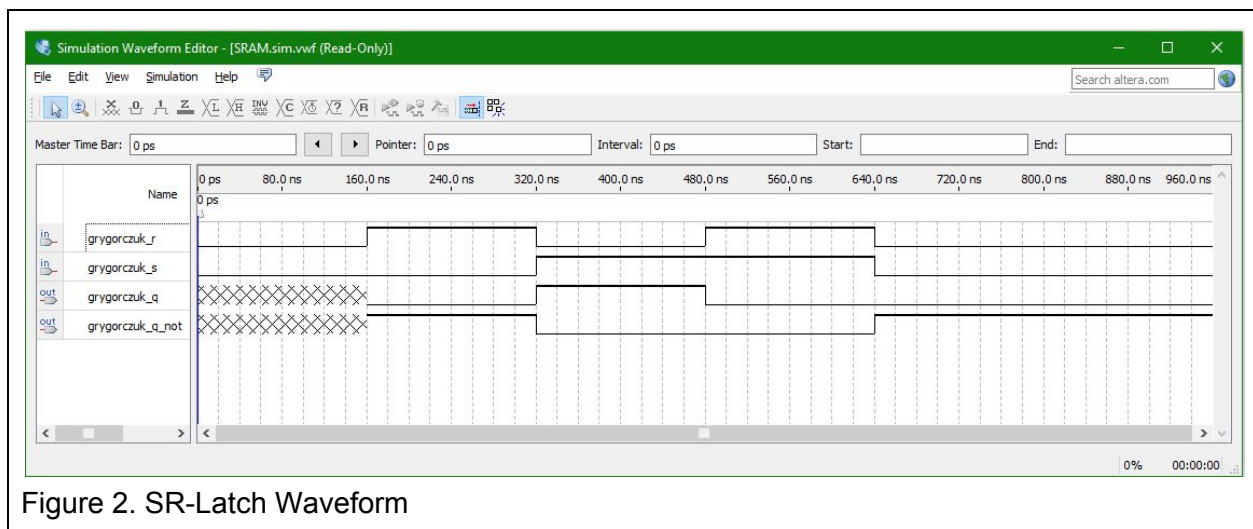


Figure 2. SR-Latch Waveform

As seen in Figure 2, when the first input is both zeros then the output is unknown, then it processed as expected till both inputs are one giving us an output of both zeroes yet when the next input is both zeroes the output is different, this is the reason why SR-Latch is inadequate for precise usage, we just don't know what could happen when both S and R are set to one. Lastly we see that the SR-Latch holds onto the value in the very last segment as intended serving as a basic memory unit.

## Control SR-Latch

Next we look at a Control SR-Latch, it's an improvement on the SR-Latch in the sense that it gives us more control over when the state can change however it's still has the issue of when both S and R are set to 1 we have an undefined state. Below is the block diagram implementation and waveform of the Control SR-Latch

C	S	R	Q	Q'	State
0	X	X	Q	Q'	No Change
1	0	0	Q	Q'	No Change
1	0	1	0	1	Reset
1	1	0	1	0	Set
1	1	1	?	?	Undefined

Tabel 2. Control SR-Latch

The X in S and R rows means that no matter what state S or R is the it all depends on C.

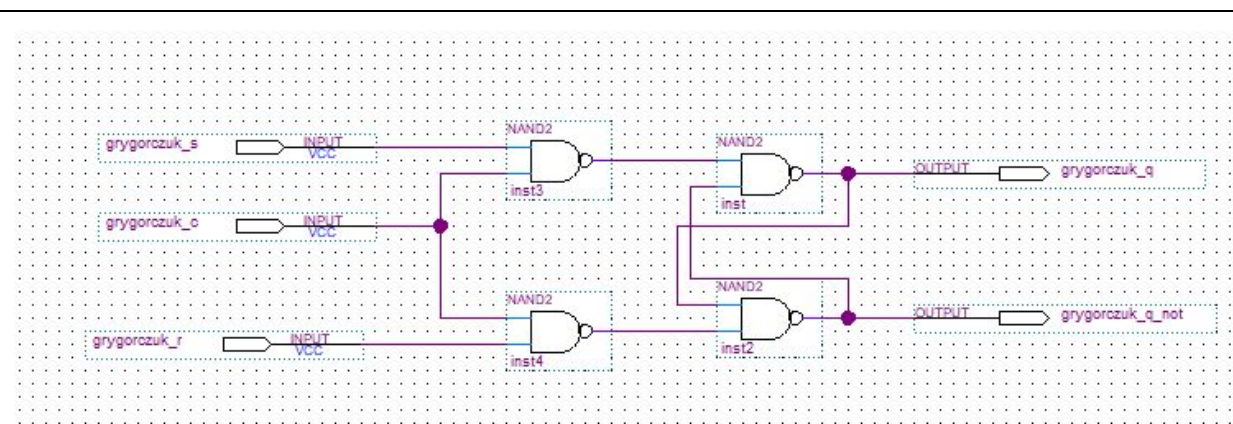


Figure 3. Control SR-Latch

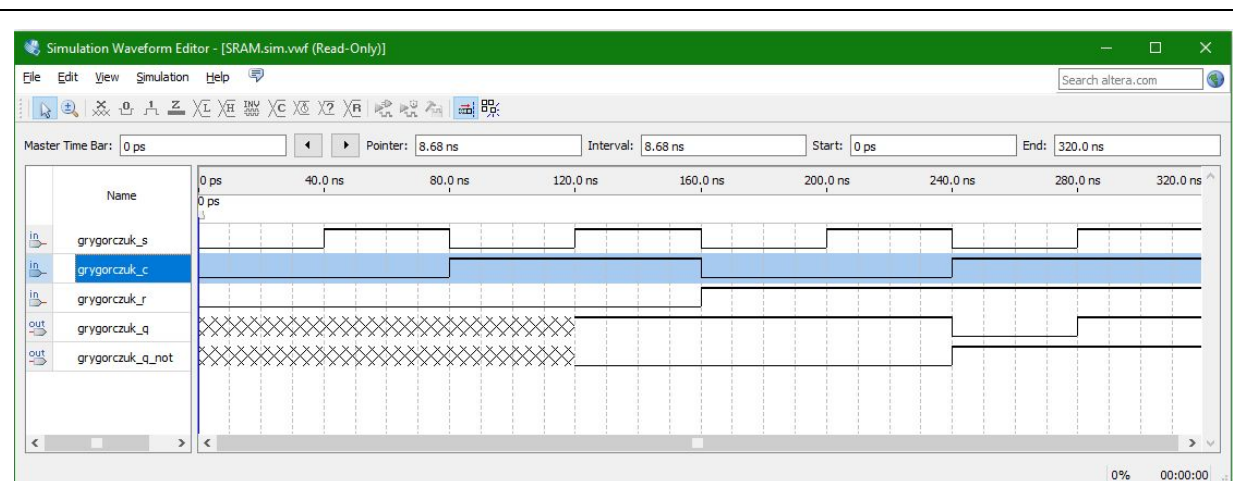



Figure 4. Control SR-Latch Waveform

## D-Latch

C	D	Q	Q'	State
0	X	Q	Q'	No Change
1	0	0	1	Reset
1	1	1	0	Set

The diagram shows a logic circuit for a 2-bit adder. It has two inputs, `grygorczuk_d` and `grygorczuk_c`, each connected to an inverter (labeled `inst1` and `inst3` respectively). The circuit uses four NAND gates (labeled `inst2`, `inst3`, `inst4`, and `inst5`) and two output buffers (labeled `OUTPUT`). The inputs are connected to the NAND gates as follows: `grygorczuk_d` and `grygorczuk_c` are connected to the inputs of `inst2` and `inst3`. The outputs of `inst2` and `inst3` are connected to the inputs of `inst4` and `inst5`. The outputs of `inst4` and `inst5` are connected to the `OUTPUT` buffers, which produce the final outputs `grygorczuk_a` and `grygorczuk_a_not`.

5

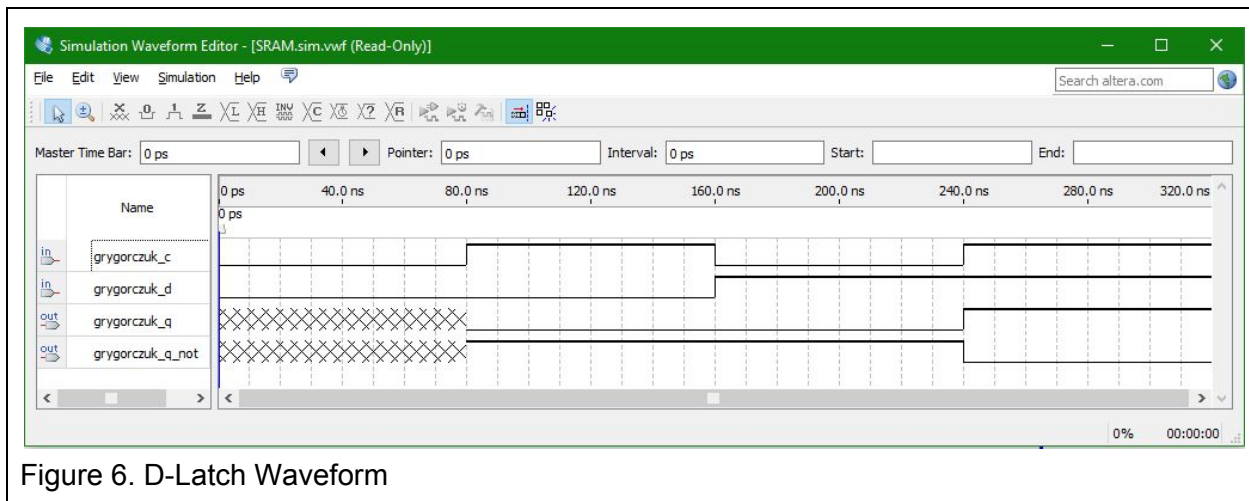


As seen above first the D-Latch holds the state, the sets it to Reset, holds it and then sets it to Set. There is no issue of having unknown outputs once the memory has been set.


## Master Slave Flip Flop:

Now that we have a reliable memory device we have to make sure that it grabs the right data at the right time and not any random data that might come its way. The solution to that is the Master Slave Flip Flop which will only change states during the rising edge in our situation, meaning that whatever the state D is it will be saved if the clock is going from low to high state.

C	D	State
Low to High	X	Change
High to Low	X	No Change

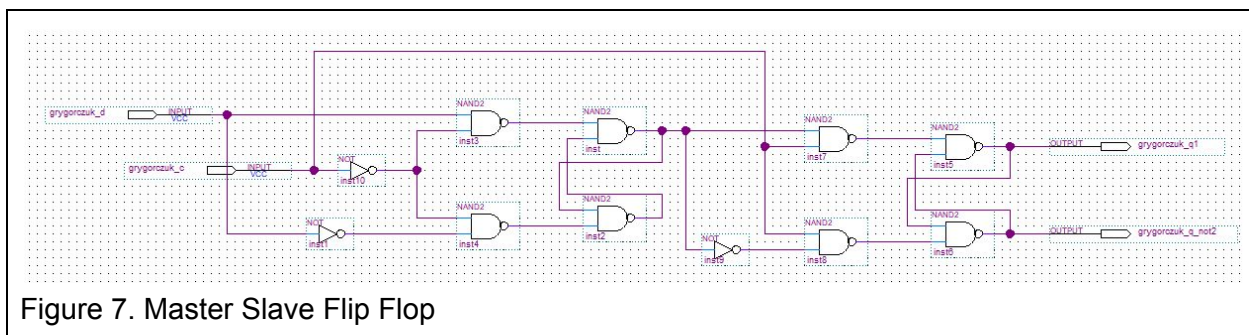Tabel 4. Master Slave Flip Flop Truth Table



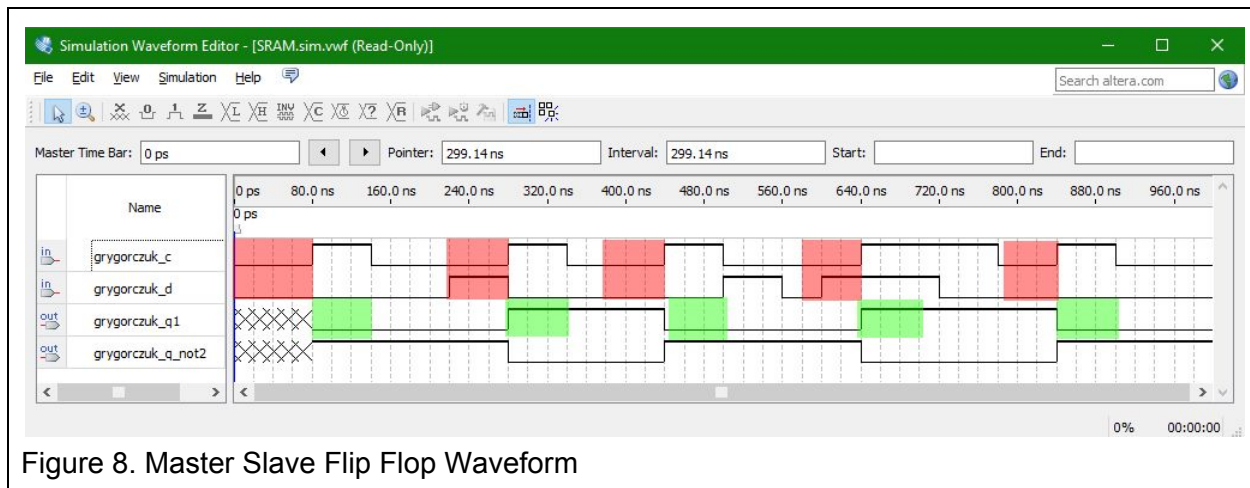

In figure 8 we look at a random wavepatter given to C and D. As we can see Q becomes whatever whatever D was before the C went from low to high. I highlighted the rising edge moments in red and the saved data after in green to show that it indeed saves the data from the previous period of rising edge. Everywhere else there is no change occuring.

## SRAM:

Now that the basics are complete it's time to build the SRAM, we will have to do few things to get there, build a single cell of an SRAM, create a 16x1 SRAM module, create an address decoder which will allow us to switch between sixteen different SRAM locations, put all of that together to create a 16x4 SRAM, and finally create a decoder for a seven segment display.

### SRAM Cell:

To create an SRAM Cell we will use the Master Slave Flip Flop we showed in previous section with the addition of new inputs that will serve as our C and D. We will have Input, Select Chip, and Write Enable. Input is straightforward it's the data we are trying to save. Select Chip will make the device operational, if it's high it will save, if it's low it will make the device give out a buffer state. The Write Enable allows data from the Input to be saved.

Select Chip	Write Enable	Input	State
0	X	X	Z
1	0	X	Output
1	1	X	Output and Save

Tabel 5. SRAM Cell



When both Select Chip is 0, Write Enable can be either 0 or 1 the output will only give out the buffer Z. If Select Chip is 1 and Write Enable is 0 the output will be whatever is stored in the SRAM Cell. If both the Select Chip and Write Enable are on it will give the output and save the input.

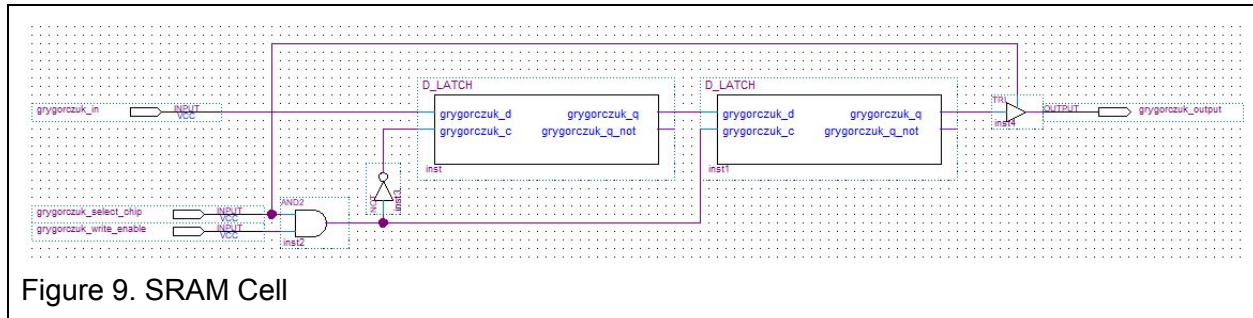


Figure 9. SRAM Cell

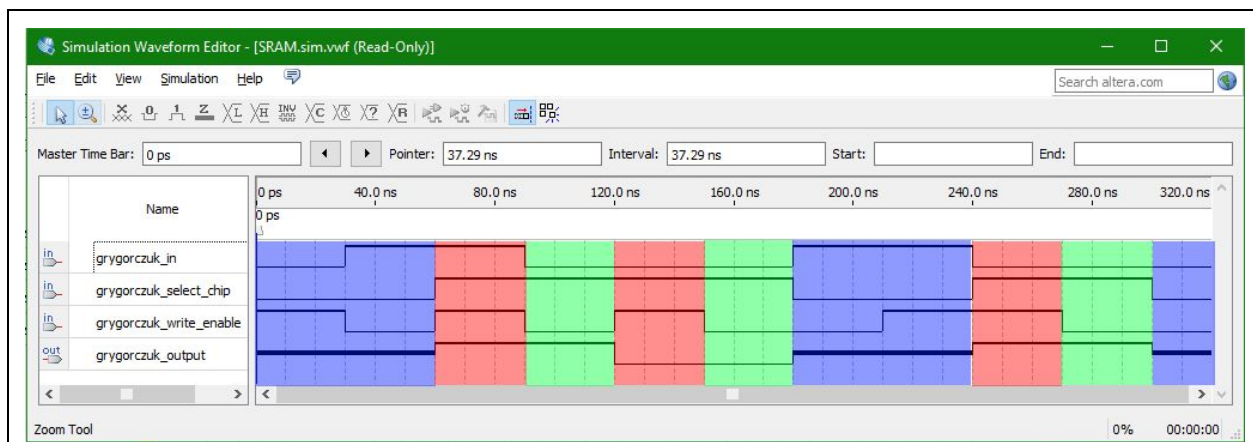


Figure 10. SRAM Cell Waveform

In figure 10 I show that when Select Chip is 0 the output is the buffer Z in blue. That when both Select chip and Write Enable are on they save and display the value of input of the value that it was during the rising edge in red and in green I show when only Select Chip is 1 it displays the stored value.

## SRAM 16x1 Module:

Next step to getting a SRAM that is 16x4 is to make a 16x1 modula that will help make the job easier. The modula will have three inputs, the address decoder value which will tell the module which of the cells to read/write from (This is the Select Chip for a Cell). Only the chosen cell will have some kind of output all the others will give off the Z buffer. The input that will be stored in the chosen cell, and the write enable which will say that you can overwrite what's inside the cell. It will have output which take the output from chosen cell and pass it onto the seven segment display. Below are the block diagram of the Module and a waveform showing how it functions.

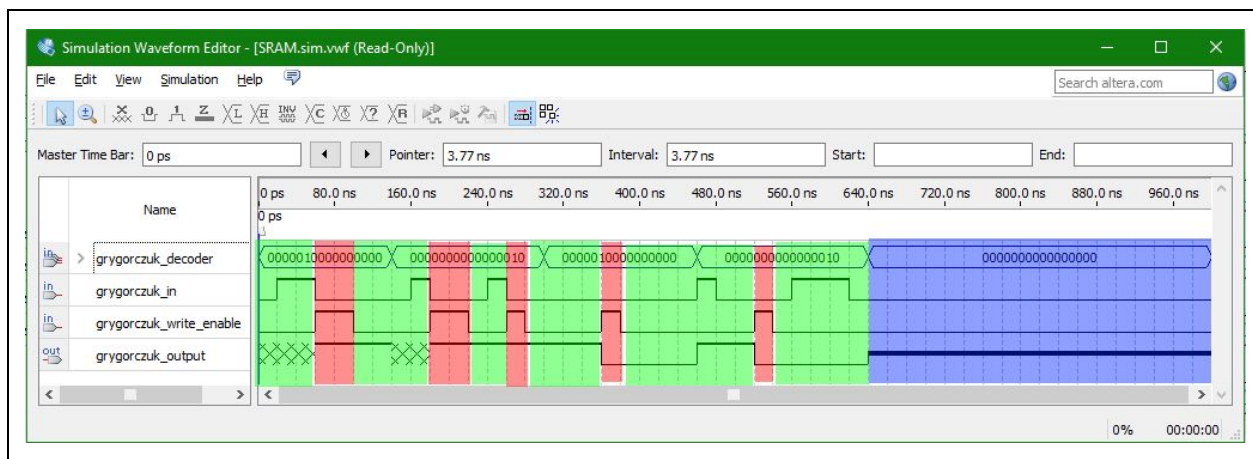
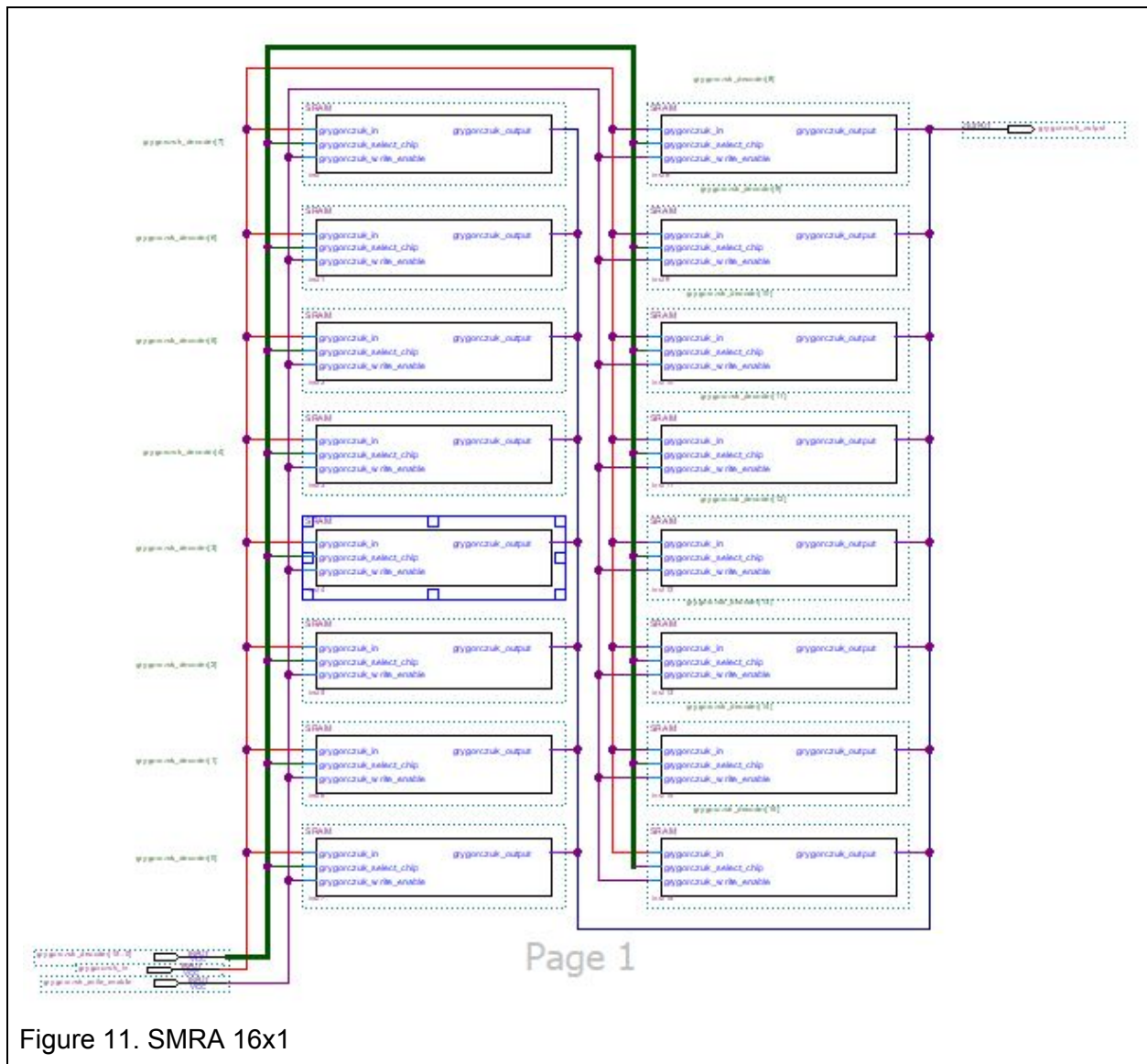


Figure 12. SRAM 16x1 Waveform

In Figure 12, we see that we can access any of that 16 cells using the decoder input, you see me access 10th cell and the 2nd cell multiple time save and read their values they had every time the waveform is red. Anytime the waveform is green its us accessing the cell to read from it and anytime the input from the decoder is all zeroes the output will give us the buffer signal. This works exactly like a Master Slave Flip Flop but now we can acesse many of them not just one.

## Address Decoder:

To be able to switch between the different cells we need a easy way to do so, we want to use only four inputs since that gives us sixteen options, so we create a four to sixteen decoder, shown in the code below.

```
library ieee;
use ieee.std_logic_1164.all;

entity decoder_four_to_sixteen is
    port(
        grygorczuk_address: in std_logic_vector(3 downto 0);
        grygorczuk_decoder_output : out std_logic_vector(15 downto 0)
    );
end decoder_four_to_sixteen;

architecture decoder_four_to_sixteen_logic of decoder_four_to_sixteen is

begin

    with grygorczuk_address select
        grygorczuk_decoder_output <= "0000000000000001" when "0000",
        "0000000000000010" when "0001",
        "0000000000000100" when "0010",
        "0000000000000100" when "0011",
        "0000000000001000" when "0100",
        "0000000000100000" when "0101",
        "0000000001000000" when "0110",
        "0000000010000000" when "0111",
        "0000000100000000" when "1000",
        "0000001000000000" when "1001",
        "0000010000000000" when "1010",
        "0000100000000000" when "1011",
        "0001000000000000" when "1100",
```

"0010000000000000" when "1101",  
 "0100000000000000" when "1110",  
 "1000000000000000" when "1111",  
 "0000000000000000" when others;

end decoder\_four\_to\_sixteen\_logic;

Code 1. Four to Sixteen Decoder

This code will allow us to use four switches to access sixteen different SRAM cells.



Figure 13. Four to Sixteen Decoder

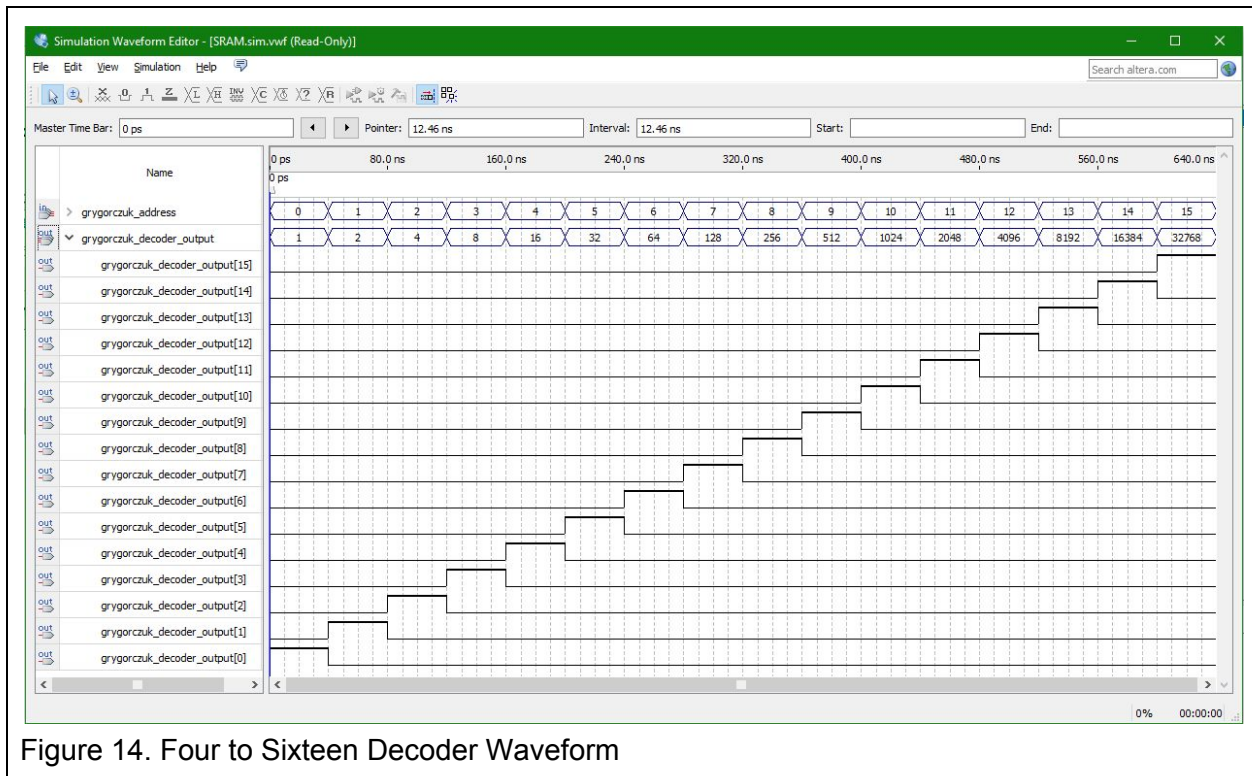


Figure 14. Four to Sixteen Decoder Waveform



## SRAM 16x4:

Once we have the decoder and the SRAM 16x1 completed we can put the two together to create the SRAM 16x4. This will allow us to store an array of four bits, and recall that array at any moment. Let's look over the inputs we have now, there's the four bits of input that will be stored in the four SRAM cells, there the four bit address operation code which selects which row of the cells to save/read the input from/to. There is the Write Enable that lets the chips save the input. The Select Chip which works in conjunction to the write enable. And finally there is the output enable which allows the output to be sent from the SRAM to some other component. Below is the block diagram and the waveform that show its functionality.


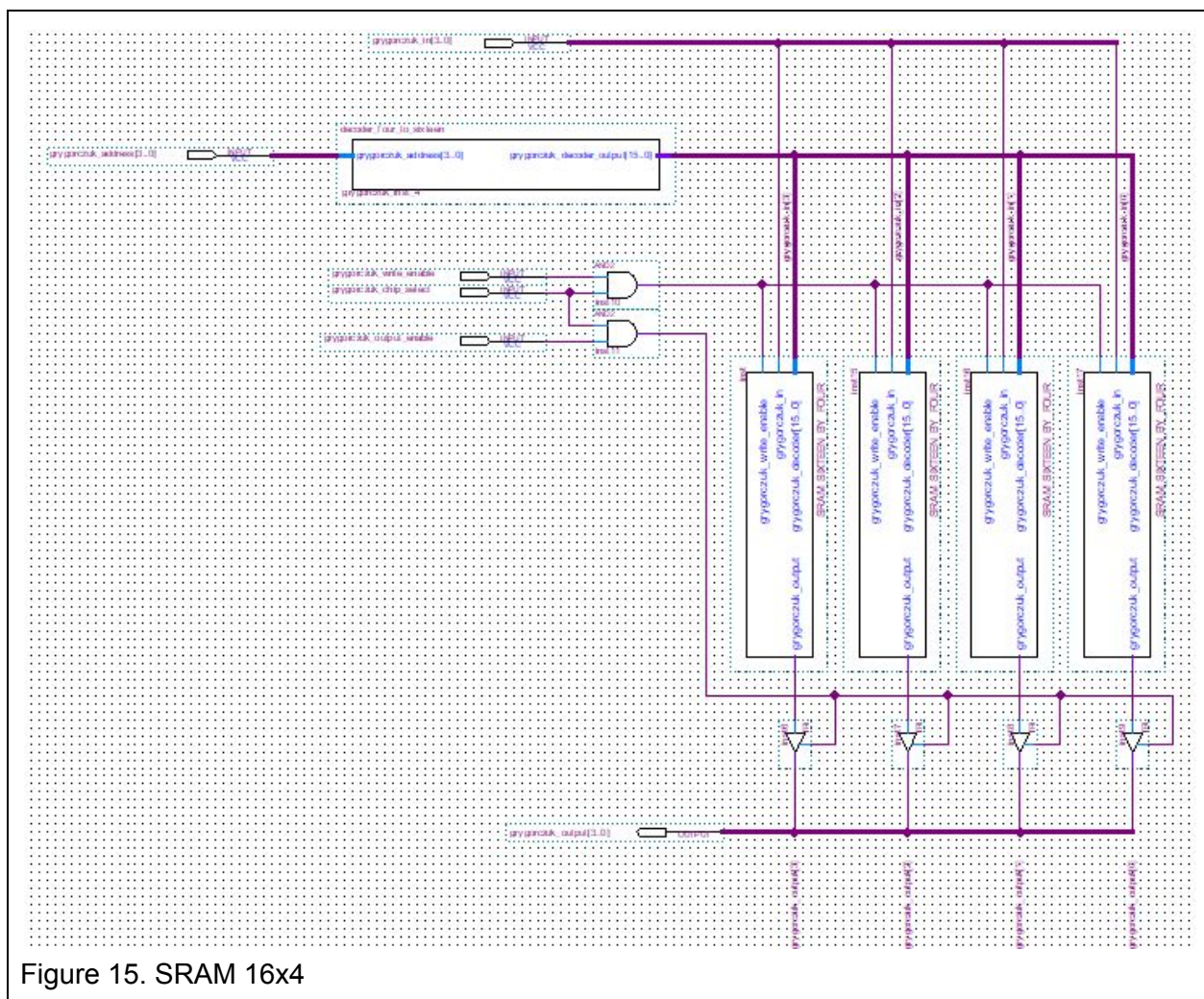


Figure 15. SRAM 16x4

 As shown in Figure 13, the system takes zeroth bit from the left and the nth bit from the right, n being third in this case.



In Figure 16 you can see all the times that the memory gets saved in red, any time it's being displayed in green. Anytime the buffer is on because the Chip Select is off in dark blue, anytime it's off because the output enable is off in yellow and teal when both Chip Select and Output Enable are off.

In Figure 16, I access two different rows, 4 and 7 and I save different values into them and read them without modifying the memory stored. It works just like a Master Slave Flip Flop but with four different cells assessed at the same time and with ability to choose an array of cells.

## Seven Segment Display:

Next we had to create a way to display the results of these actions on the board, we are going to do that by displaying them on a seven segment display in hexadecimal. Below is the code used to do that.

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_arith.all;
use ieee.std_logic_unsigned.all;

entity decoder_and_seven_segment_display is
    port(
        grygorczuk_input: in std_logic_vector(3 downto 0);
        grygorczuk_a, grygorczuk_b, grygorczuk_c, grygorczuk_d, grygorczuk_e, grygorczuk_f, grygorczuk_g: out
        std_logic
    );
end decoder_and_seven_segment_display;

architecture decoder_and_seven_segment_display_logic of decoder_and_seven_segment_display is
    signal grygorczuk_data : std_logic_vector(6 downto 0);
begin
    process (grygorczuk_input)
    begin
        case grygorczuk_input is
            when "0000" =>
                grygorczuk_data <= "0000001";
            when "0001" =>
                grygorczuk_data <= "1001111";
            when "0010" =>
                grygorczuk_data <= "0010010";
```

```

        when "0011" =>
            grygorczuk_data <= "0000110";
        when "0100" =>
            grygorczuk_data <= "1001100";
        when "0101" =>
            grygorczuk_data <= "0001000";
        when "0110" =>
            grygorczuk_data <= "0100000";
        when "0111" =>
            grygorczuk_data <= "0001111";
        when "1000" =>
            grygorczuk_data <= "0000000";
        when "1001" =>
            grygorczuk_data <= "0001100";
        when "1010" =>
            grygorczuk_data <= "0001000";
        when "1011" =>
            grygorczuk_data <= "1100000";
        when "1100" =>
            grygorczuk_data <= "0110001";
        when "1101" =>
            grygorczuk_data <= "1000010";
        when "1110" =>
            grygorczuk_data <= "0110000";
        when "1111" =>
            grygorczuk_data <= "0111000";
        when others =>
            NULL;
    end case;
end process;

grygorczuk_a <= grygorczuk_data(6);
grygorczuk_b <= grygorczuk_data(5);
grygorczuk_c <= grygorczuk_data(4);
grygorczuk_d <= grygorczuk_data(3);
grygorczuk_e <= grygorczuk_data(2);
grygorczuk_f <= grygorczuk_data(1);
grygorczuk_g <= grygorczuk_data(0);

```

end decoder\_and\_seven\_segment\_display\_logic;

## Code 2. Seven Segment Display

ABCDEFG	Seven Segment Display
0000001	0
1001111	1
0010010	2
0000110	3
1001100	4
0001000	5

0100000	6
0001111	7
0000000	8
0001100	9
0001000	A
1100000	b
0110001	C
1000010	D
0110000	E
0111000	F

Tabel 6. Seven Segment Hexadecimal

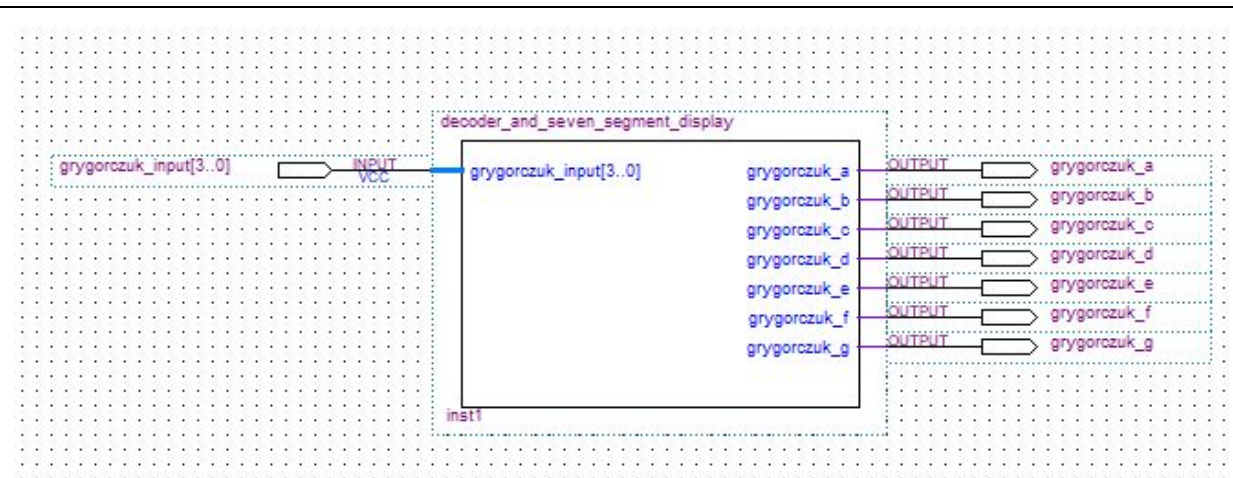


Figure 17. Seven Segment Display



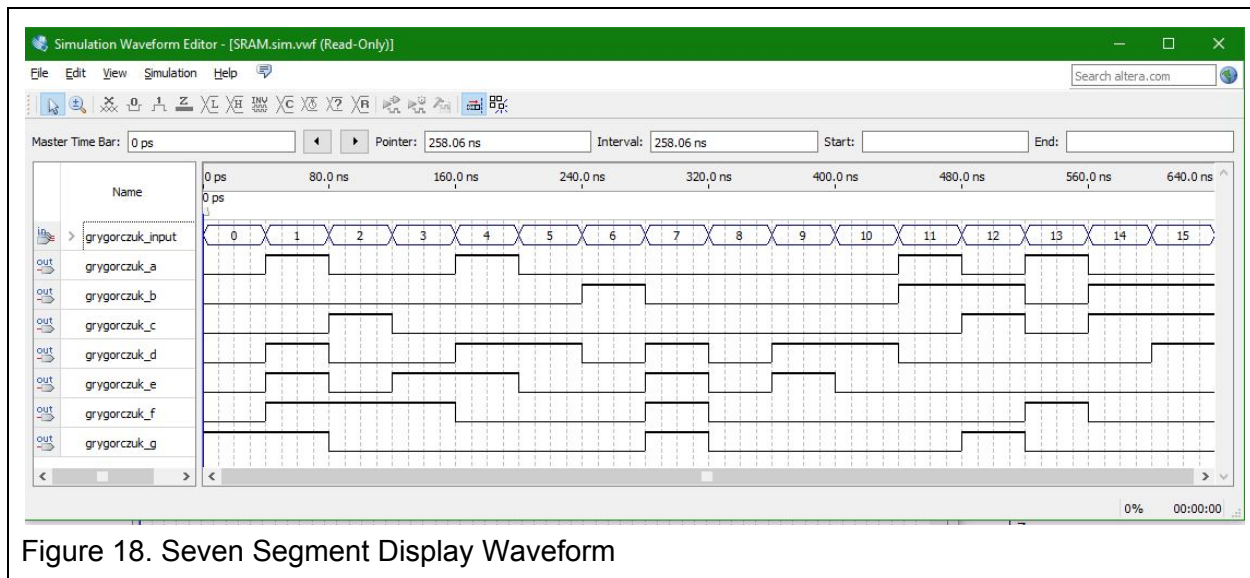


Figure 18. Seven Segment Display Waveform

You can compare Figure 18 to Table 6 to see that the outputs are giving out appropriate symbols to the seven segment display.

## SRAM 16x4 and 16x8 With Seven Segment Display:

Below is what one SRAM 16x4 looks like when set up to the seven segment display.


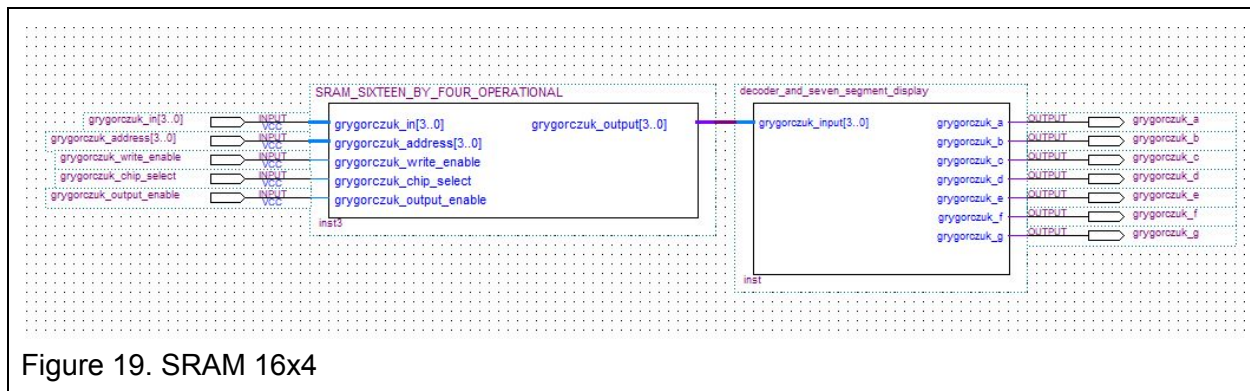



Figure 19. SRAM 16x4

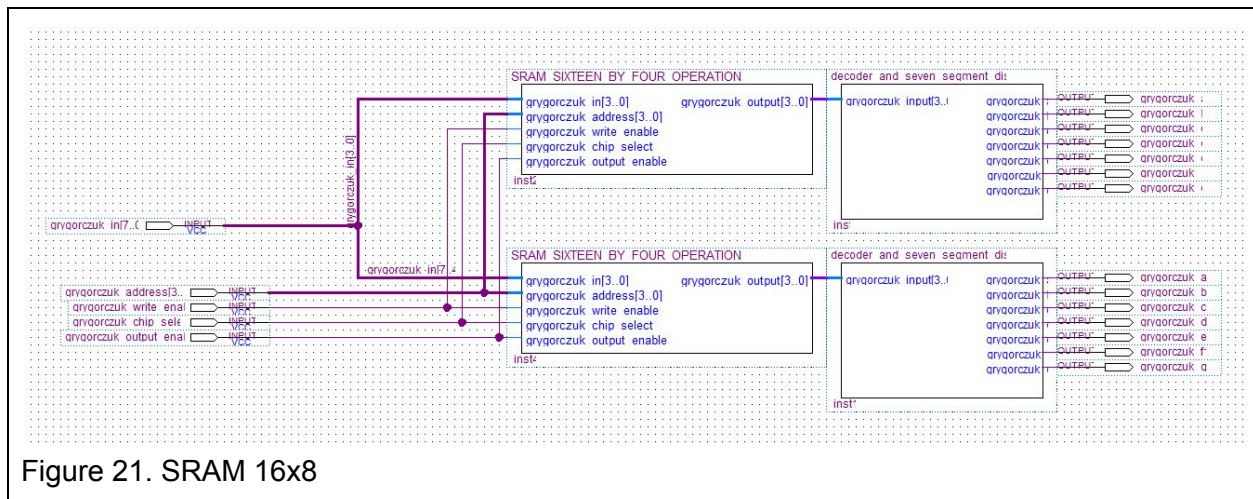Next step we take to build up towards SRAM 16x32 is we take two of these SRAM 16x4 to make a 16x8. Shown below


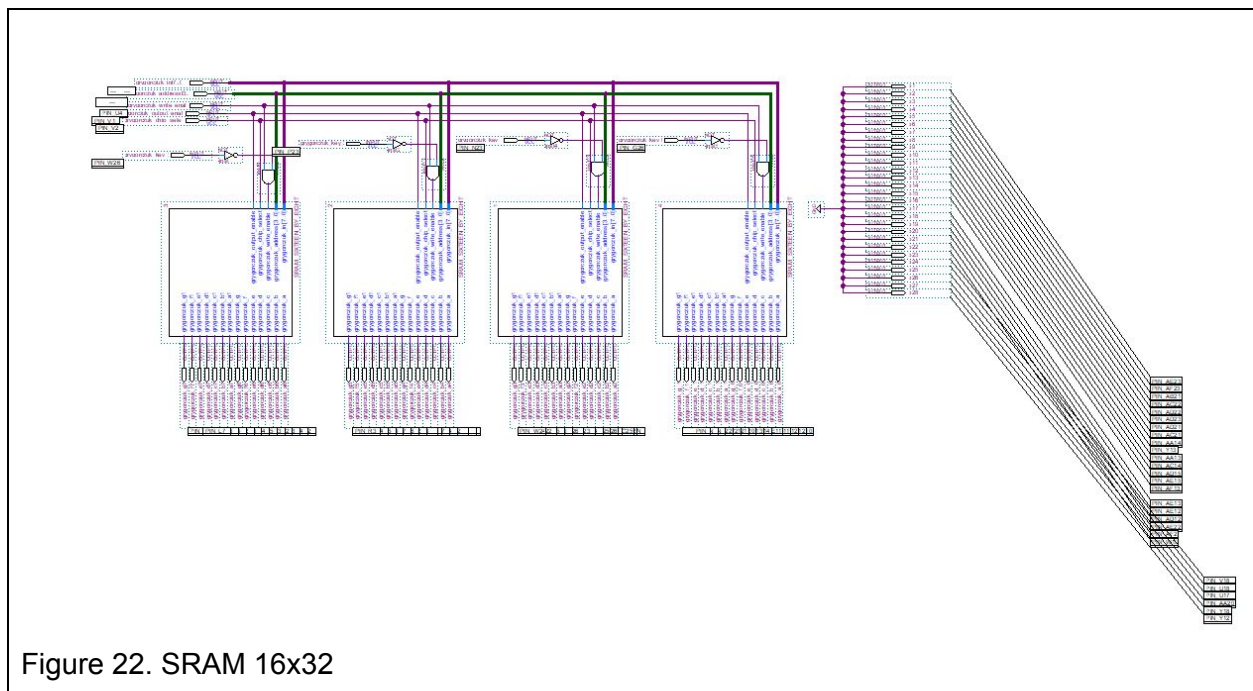
## SRAM 16x32:

Once I have the 16x8 I use four of those to create the final build of the 16x32. Since we have such a large number of bits to be placed we're going to save them eight bits at a time. To do this I've set up signals for the keys and when the key is pressed and write enable is on it will write to the 0-7 range, 8-15 range, 16-23 range, and 24-31 range. The outputs on the side is to make sure that the LEDs are off during the program's run time.



## Pinouts

To, Location

grygorczuk\_in[0], PIN\_N25  
grygorczuk\_in[1], PIN\_N26  
grygorczuk\_in[2], PIN\_P25  
grygorczuk\_in[3], PIN\_AE14  
grygorczuk\_in[4], PIN\_AF14  
grygorczuk\_in[5], PIN\_AD13  
grygorczuk\_in[6], PIN\_AC13  
grygorczuk\_in[7], PIN\_C13

grygorczuk\_key\_0, PIN\_G26  
grygorczuk\_key\_1, PIN\_N23  
grygorczuk\_key\_2, PIN\_P23  
grygorczuk\_key\_3, PIN\_W26

grygorczuk\_address[0], PIN\_B13  
grygorczuk\_address[1], PIN\_A13  
grygorczuk\_address[2], PIN\_N1  
grygorczuk\_address[3], PIN\_P1

grygorczuk\_write\_enable, PIN\_U4  
grygorczuk\_chip\_select, PIN\_V2  
grygorczuk\_output\_enable, PIN\_V1

grygorczuk\_a\_0, PIN\_AF10  
grygorczuk\_b\_0, PIN\_AB12  
grygorczuk\_c\_0, PIN\_AC12  
grygorczuk\_d\_0, PIN\_AD11  
grygorczuk\_e\_0, PIN\_AE11  
grygorczuk\_f\_0, PIN\_V14  
grygorczuk\_g\_0, PIN\_V13

grygorczuk\_a\_1, PIN\_V20  
grygorczuk\_b\_1, PIN\_V21  
grygorczuk\_c\_1, PIN\_W21  
grygorczuk\_d\_1, PIN\_Y22  
grygorczuk\_e\_1, PIN\_AA24  
grygorczuk\_f\_1, PIN\_AA23  
grygorczuk\_g\_1, PIN\_AB24

grygorczuk\_a2, PIN\_AB23  
grygorczuk\_b2, PIN\_V22  
grygorczuk\_c2, PIN\_AC25  
grygorczuk\_d2, PIN\_AC26  
grygorczuk\_e2, PIN\_AB26  
grygorczuk\_f2, PIN\_AB25  
grygorczuk\_g2, PIN\_Y24

grygorczuk\_a3, PIN\_Y23  
grygorczuk\_b3, PIN\_AA25  
grygorczuk\_c3, PIN\_AA26  
grygorczuk\_d3, PIN\_Y26  
grygorczuk\_e3, PIN\_Y25  
grygorczuk\_f3, PIN\_U22  
grygorczuk\_g3, PIN\_W24

grygorczuk\_a4, PIN\_U9  
grygorczuk\_b4, PIN\_U1  
grygorczuk\_c4, PIN\_U2  
grygorczuk\_d4, PIN\_T4  
grygorczuk\_e4, PIN\_R7  
grygorczuk\_f4, PIN\_R6

grygorczuk\_g4, PIN\_T3

grygorczuk\_a5, PIN\_T2  
grygorczuk\_b5, PIN\_P6  
grygorczuk\_c5, PIN\_P7  
grygorczuk\_d5, PIN\_T9  
grygorczuk\_e5, PIN\_R5  
grygorczuk\_f5, PIN\_R4  
grygorczuk\_g5, PIN\_R3

grygorczuk\_a6, PIN\_R2  
grygorczuk\_b6, PIN\_P4  
grygorczuk\_c6, PIN\_P3  
grygorczuk\_d6, PIN\_M2  
grygorczuk\_e6, PIN\_M3  
grygorczuk\_f6, PIN\_M5  
grygorczuk\_g6, PIN\_M4

grygorczuk\_a7, PIN\_L3  
grygorczuk\_b7, PIN\_L2  
grygorczuk\_c7, PIN\_L9  
grygorczuk\_d7, PIN\_L6  
grygorczuk\_e7, PIN\_L7  
grygorczuk\_f7, PIN\_P9  
grygorczuk\_g7, PIN\_N9

o1, PIN\_AE23  
o2, PIN\_AF23  
o3, PIN\_AB21  
o4, PIN\_AC22  
o5, PIN\_AD22  
o6, PIN\_AD23  
o7, PIN\_AD21  
o8, PIN\_AC21  
o9, PIN\_AA14  
o10, PIN\_Y13  
o11, PIN\_AA13  
o12, PIN\_AC14  
o13, PIN\_AD15  
o14, PIN\_AE15  
o15, PIN\_AF13  
o17, PIN\_AE13  
o18, PIN\_AE12  
o19, PIN\_AD12  
o20, PIN\_AE22  
o21, PIN\_AF22  
o22, PIN\_W19  
o23, PIN\_V18  
o24, PIN\_U18  
o25, PIN\_U17  
o26, PIN\_AA20  
o27, PIN\_Y18  
o28, PIN\_Y12

Code. Pin Out

## Conclusion:

This project showed basic memory can be created and how you can access and store the bits at different addresses with the help of two D-Latches set up in a Master Slave Flip Flop. It showed the difference between a Latch and a Flip Flop, where the first changes state based on current state, high or low, while the other changes state based on rising or falling edge. It also challenged us to create a interesting way to store bytes using a limited input space having to use only eight inputs to dictate thirty two outputs that are started on the SRAM 16x32.